

# BOOLEAN LOGIC IMPLEMENTATION BY USING ARDUINO WITH AVR ASSEMBLY

GADDAM LIKHITHESHWAR

glikhitheshwar@gmail.com

FWC220099 IITH-Future Wireless Communications Assignment-1

## Contents

- 1 Abstract
- 2 Components
- 3 BooleanEquation
- 4 Hardware Connections
- 5 Procedure
- 6 Truth table for given K-map
- 7 Software

## 1 Abstract

This manual shows Realisation of boolean expression from the given k-map by using arduino with AVR ASSEMBLY

## 2 Components

Component	Value	Quantity
Arduino	UNO	1
Bread board	-	1
Jumper wires	M-M	8
Led	-	1
Resistor	150ohms	1

## 3 BooleanEquation

- 1 By using boolean equation we write our code in assembly we get the boolean equation as follows

1  $Y = QR' + S$

## 4 Hardware Connections

- 1 1.in arduino we are having pins P,Q,R,S.here we are using port B pin 8 is taken as output pin.
- 2 2.port D pins 2,3,4,5 pins are taken as a inputs. portD pins 2,3,4,5 pins are connected vcc or gnd in breadboard as per truth table

## 5 Procedure

- 1) Connect 5v of the Arduino to the top red of the bread board and GND to the bottom green
- 2) Connect b0 pin in the arduino to connect to one LED+
- 3) Connect arduino d2 pin to the gnd or vcc according to inputs
- 4) Connect arduino d3 pin to the gnd or vcc according to inputs
- 5) Connect arduino d4 pin to the gnd or vcc according to inputs
- 6) Connect arduino d5 pin to the gnd or vcc according to inputs
- 6) Connect one LED+ to one end of the resistor and other end of resistor to vcc and gnd the

other terminal of LED

7) Change the d2 d3 d4 d5 pins in the arduino from vcc to gnd as per truthtable and observe the outputs

## 6 Truth table for given K-map

P	Q	R	S	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

TABLE 1

## 7 Software

Execute the following code using the below provided link.

<https://github.com/likhith1101/fwcassgn>